



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรชูปเปอร์ไซเรน พลังสูง 10 วัตต์
SUPER SIREN 10W

CODE 230

LEVEL1

วงจรชูปเปอร์ไซเรนพลังสูงชุดนี้ เหมาะสำหรับที่จะนำไปใช้เป็น
วงจรเตือนภัยหรือนาฬิกาดิจิตอลยนต์ได้

ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 12 โวลต์ดีซี
- กินกระแสสูงสุดประมาณ 200 มิลลิแอมป์
- ให้กำลังเสียง 10 วัตต์ ที่ลำโพง 8 โอห์ม
- ความดังประมาณ 108 dB/m.
- ขนาดแพนวงจรพิมพ์ : 2.15 x 1.41 นิ้ว

การทำงานของวงจร

TR1 และ TR2 จะถูกต่อเป็นวงจรกำเนิดความถี่ต่ำ โดยความถี่ต่ำนี้จะขึ้นอยู่กับ R1, R2, R3, C1, C2 โดยความถี่นี้จะส่งออกทางขา E ของ TR2 โดยมี R4 ต่อลงกราวน์และมี C3 ทำหน้าที่ทำให้เกิดทางเสียง ของความถี่ต่ำ ที่ขา E ของ TR2 จะต่อผ่าน R7, R8 ไปเข้าชุดกำเนิดความถี่สูง ซึ่งประกอบด้วย TR3, TR4, R5, R7, R8, R9, C4, C5 ความถี่สูงที่ถูกควบคุมจะส่งผ่านทาง R6 เข้าขา B ของ TR ซึ่งเป็นทรานซิสเตอร์ เพื่อทำการขยายออกลำโพงต่อไป

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกแสดงไว้ในรูปที่ 2 ใน การประกอบวงจรควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวต้านทานและໄ่ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ เช่น ไดโอด, แคปซิลเตอร์แบบบอเล็กทรอนิกส์และทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบของวงจรก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ขั้วที่แผ่นวงจรพิมพ์กับตัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับข้ามแล้ว อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูขั้วและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และ ในการบัดกรีให้ใช้หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตัวบัดกรีที่มีอัตราส่วนของดินสูก และตะกั่วอยู่ระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ภายในตะกั่วด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง เพื่อให้เกิดความมั่นใจแก่ตัวเราเอง แต่ถ้าเกิดใส่อุปกรณ์ผิดตำแหน่ง ควรใช้ที่ดูดตะกั่วหรือลวดซับตะกั่วเพื่อป้องกันความเสียหายที่อาจจะเกิดกับลายวงจรพิมพ์ได้

การทดสอบ

ให้ทำการต่ออุปกรณ์ต่างๆ ตามรูปที่ 3 โดยขั้วบวกต่อที่ +12V ขั้วลบต่อที่ G ลำโพงต่อที่จุด SP ลำโพงที่ใช้ควรใช้ลำโพงหรือ ขนาด 8 โอห์ม 15 วัตต์ เมื่อต่อเสร็จจะได้ยินเสียงไซเรนออกทางลำโพง หากนำไปต่อไฟบ้าน จะต้องใช้อแดปเตอร์ขนาด 800 มิลลิแอมป์ขึ้นไป

วงจรชูปเปอร์ไซเรน พลังสูง 10 วัตต์

SUPER SIREN 10W

CODE 230

LEVEL1

The FK230 10 watts Single Tone Super Siren is constructed upon the same simple lines as the FK228 however its output transistor can handle much higher peak currents making it suitable for warning device, alarm-systems, telephone ring repeaters and doorway alarms. It may be added to personnel detectors of most types.

Technical data

- Power supply : 12VDC.
- Electric current consumption : 200mA max.
- Output power : 10W max.
- Loudspeaker connection : 8 Ohm
- IC board dimension : 2.15 in x 1.41 in

How does it work

This circuit consists of low frequency and high frequency generator respectively. The low frequency is obtained from the emitter of TR2. (grounding via R4 and C3) by connecting TR1, TR2, R1, R2, R3, C1, C2 together as shown in Fig. 1. At the same time some signal from TR2 is fed into R7, R8, TR3, TR4, R5, R9, C4 and C5 as shown in Fig. 1. The outcome which is a high frequency signal is then transferred through R6 to the base of TR5 for further amplification. This signal can be heard from the loudspeaker.

Circuit assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

This kit need an operating voltage of 12VDC. When apply this voltage by means of an adaptor (12VDC) to the circuit the siren sound will come out of the loudspeaker.

Figure 1. The super siren circuit

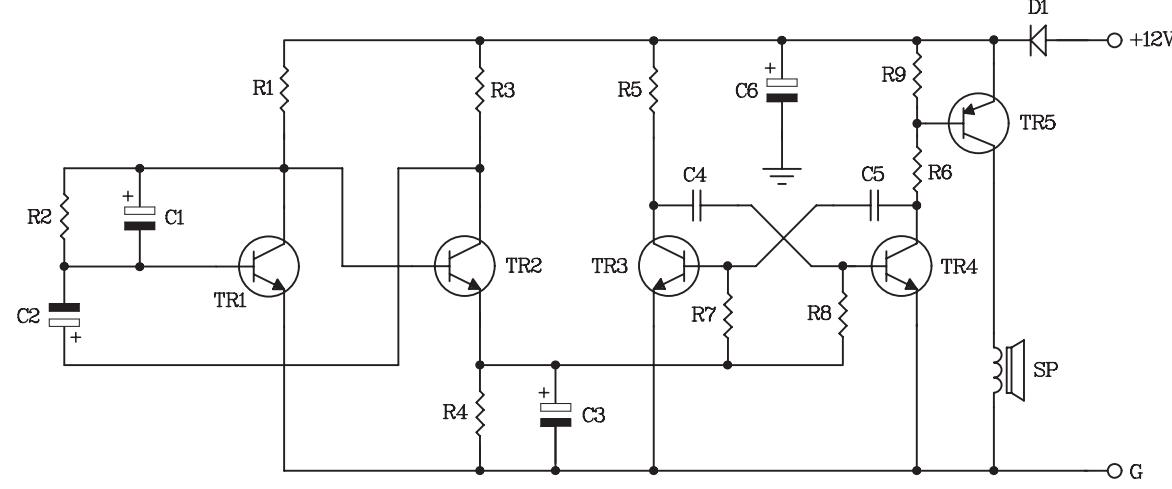


Figure 2. Circuit Assembling


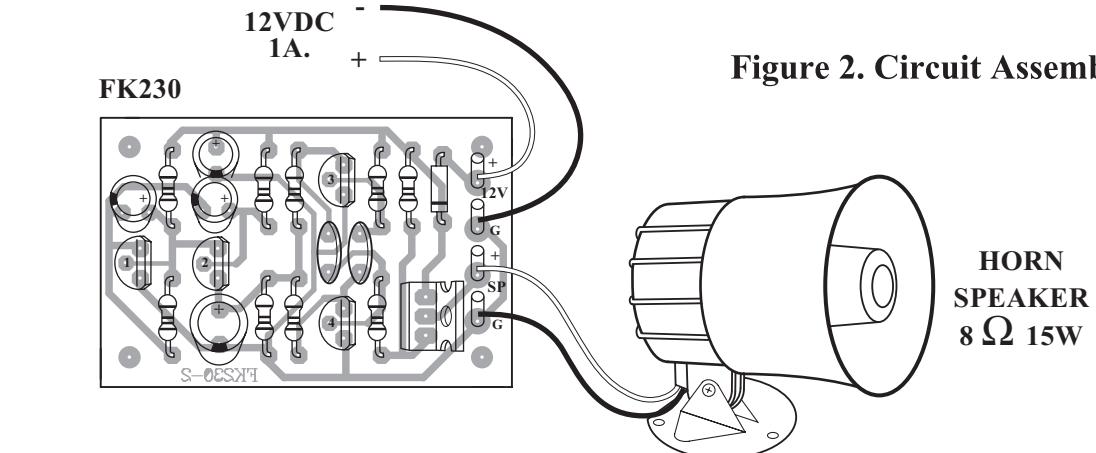


Figure 3. Installing the components

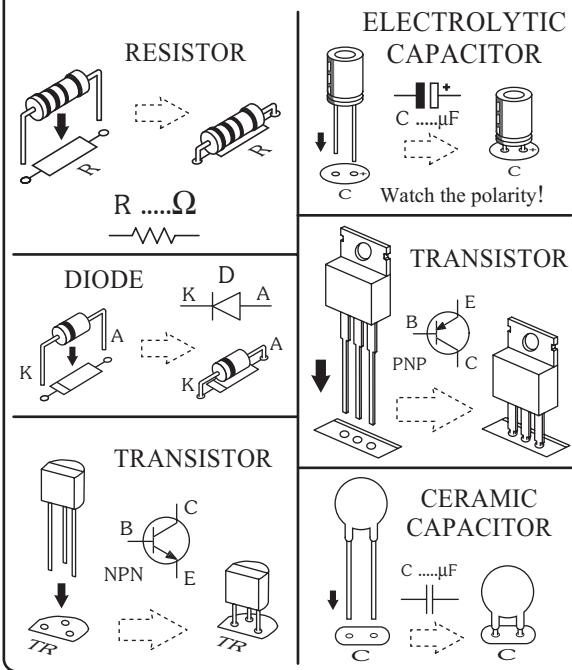

NOTE:

FUTURE BOX FB04 is suitable for this kit.