

วงจรมีเสียงเพลงจากไอซี เป็นวงจรมีกำเนิดเสียงชนิดหนึ่ง โดยเสียงเพลงที่เราได้ยินนี้ เกิดจากการเขียนโปรแกรมลงไปยังตัวไอซีไมโครคอนโทรลเลอร์ โดยวงจรมีสามารถนำไปใช้ประโยชน์ในการเล่น, เสียงเตือน, กริ่งประตูเสียงดนตรี เป็นต้น

ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 3-4.5 โวลต์ดีซี
- ที่ 3 โวลต์ดีซี ขณะทำงาน กินกระแส 85 มิลลิแอมป์
- ที่ 4.5 โวลต์ดีซี ขณะทำงาน กินกระแส 105 มิลลิแอมป์
- ที่ 3 โวลต์ดีซี ขณะสแตนด์บาย กินกระแส 60 ไมโครแอมป์
- ที่ 4.5 โวลต์ดีซี ขณะสแตนด์บาย กินกระแส 80 ไมโครแอมป์
- มีสวิทช์เลือกเสียงเพลงได้ 3 เพลง คือ Jingle Bells, It's a Small World และ Happy Birth Day
- ขนาดแผ่นวงจรพิมพ์ : 1.37 นิ้ว x 1.15 นิ้ว

การทำงานของวงจรมี

ในวงจรมีการทำงานต่างๆ ทั้งหมดจะอยู่ในตัวไอซี IC1 โดยเอาท์พุทขา 8 ของไอซีจะต่อเข้ากับขา B ของ TR1 โดยผ่าน R3 เพื่อทำการขยายสัญญาณเสียงและส่งออกไปยังลำโพงต่อไป โดยสวิทช์ S1-S3 เป็นสวิทช์เลือกเสียงเพลง

การประกอบวงจรมี

รูปการลงอุปกรณ์แสดงไว้ในรูปที่ 2 ในการประกอบวงจรมี ควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวต้านทานและไอซีความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ ควรใช้ความระมัดระวังในการประกอบวงจรมีก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ขั้วที่แผ่นวงจรพิมพ์กับตัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับขั้วแล้ว อาจจะทำให้อุปกรณ์หรือวงจรมีเสียหายได้ วิธีการดูขั้วและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 4 แล้ว ในการบัดกรีให้ใช้หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตะกั่วบัดกรีที่มีอัตราส่วนของดีบุกและตะกั่วอยู่ระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานรอยบัดกรีในตะกั่วด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง แต่ถ้ามองผิดตำแหน่ง ควรใช้ที่ดูดตะกั่วหรือลวดขั้วตะกั่ว เพื่อป้องกันความเสียหายที่อาจจะเกิดกับลายวงจรพิมพ์

การทดสอบ

ให้ต่อไฟ 4.5 โวลต์ เข้าที่จุด +4.5V ของวงจรมี ทำการกดสวิทช์ตัวใดตัวหนึ่ง เราจะได้ยินเสียงเพลงออกมาทางลำโพง วงจรมีจะให้เสียงดังไม่มากนัก ซึ่งถ้าถ่วงลง จะให้เสียงดังขึ้นอีก ในกรณีที่เสียงเพลงกำลังเล่นอยู่ ถ้ากดสวิทช์เพื่อเลือกเพลงอื่น วงจรมีจะเปลี่ยนเสียงเพลงทันที แต่ถ้ากดสวิทช์ค้างไว้ เสียงเพลงจะดังต่อเนื่องตลอดเวลาและจะไม่สามารถกดสวิทช์ตัวอื่นได้ สำหรับเสียงเพลง สามารถเลือกได้จากสวิทช์ดังนี้

- สวิทช์ S1 เป็นเสียงเพลง Jingle Bells
- สวิทช์ S2 เป็นเสียงเพลง It's a Small World
- สวิทช์ S3 เป็นเสียงเพลง Happy Birth Day

หมายเหตุ: ในกรณีที่ใช้แหล่งจ่ายไฟ 3 โวลต์ จะไม่สามารถใช้กับอ่านธรรมดาได้ จะต้องใช้กับถ่านอัลคาไลน์หรือวงจรมีเรกูเลเตอร์ 3 โวลต์ดีซีเท่านั้น

วงจรมีเสียงเพลง 3 เพลง
THREE MUSIC SONG
CODE 284

LEVEL 1

The three digitized music song are held permanently in an IC MB95F274. A transistor output amplifier drives the supplied 8 ohm 0.25W for a demanding sound suitable for toy, alarm, small bell etc.

Technical data

- Power supply : 3-4.5VDC.
- Electric current consumption at 3VDC : 85mA (working), 60mA (standby).
- Electric current consumption at 4.5VDC : 105mA (working), 80mA (standby).
- There are three switches for select the music song (Jingle Bells, It's a Small World and Happy Birth Day).
- IC board dimension : 1.37 in x 1.15 in

How does it work

The pin 8 of IC1 is connected to the base of TR1 in order to amplify a tone frequency throughout a speaker. Switch S1, S2 and S3 are used for select the music song.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 4. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.


Testing

Apply 4.5VDC power supply to +4.5V and G point of the circuit, Press only one switch, you will hear the musical sound from speaker. In case of the music is playing, if press any switch, the music will change immediately. But if press and hold the only one switch, the music will continued to play until it was released (When press and hold the switch, cannot press other the switch). For the music song, it can select by switch:

- Switch S1 is Jingle Bells song.
- Switch S2 is It's a Small World song.
- Switch S3 is Happy Birth Day song.

NOTE: In case of supply 3VDC to the circuit, the circuit cannot operate with Zine-Carbon battery. The circuit has to use with Alkaline battery or the 3VDC regulator power supply.

Figure 1.
The Three Music Song Circuit

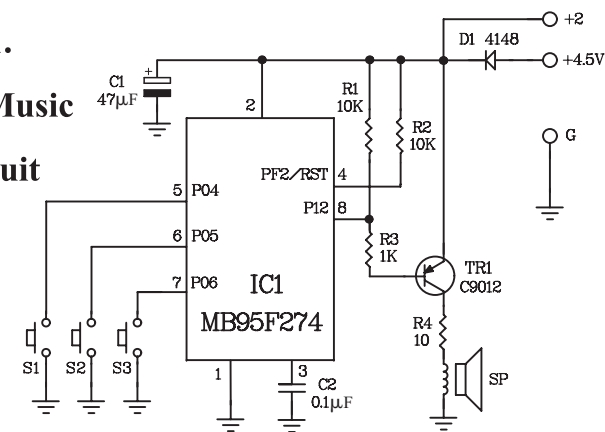

RESISTORS		
R1, R2	10kΩ	- brown-black-orange-gold
R3	1kΩ	- brown-black-red-gold
R4	10Ω	- brown-black-black-gold
ELECTROLYTIC CAPACITOR		
C1	=	47μF
CERAMIC CAPACITOR		
C2	=	104 or 0.1μF
DIODE		
D1	=	1N4148
TRANSISTOR		
TR1	=	C9012
IC		
IC1	=	MB95F274

POWER SOURCE
1.5Vx3 SIZE AA

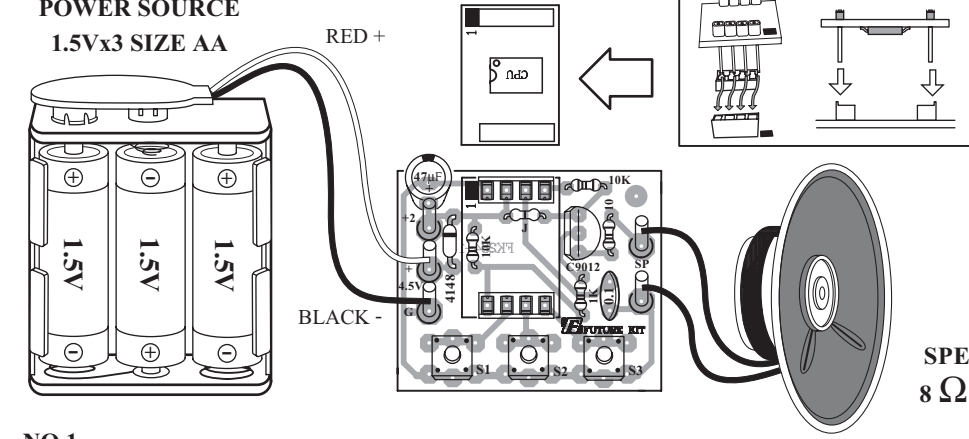


Figure 2.
Circuit Assembling (Using 4.5VDC Power Supply)

ALKALINE BATTERY x 2
SIDE AA

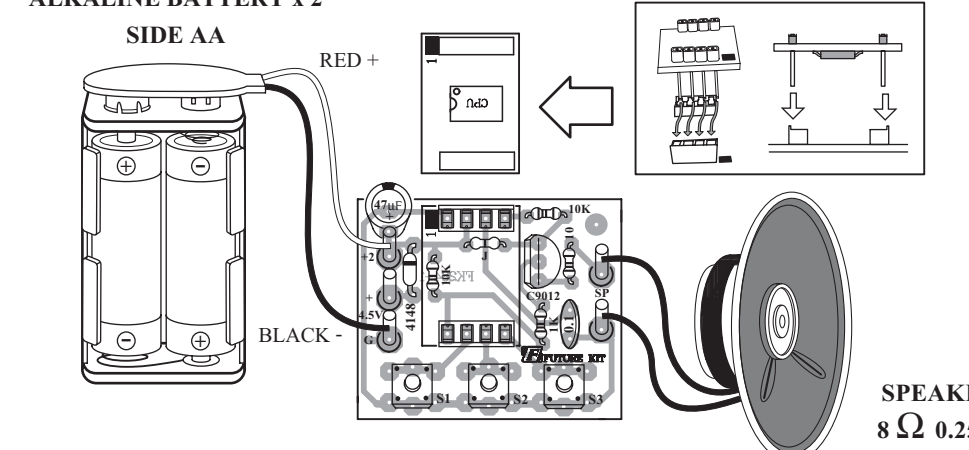


Figure 3.
Circuit Assembling (Using 3VDC Power Supply)

NOTE:
FUTURE BOX
FB17
is suitable for
this kit.

Figure 4. Installing the components

