



# FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรปรีพรมไมค์ค่อนเดนเซอร์  
NAGAOKA  
CONDENSER MIC WITH PRE-AMP  
CODE 648

วงจรปรีพรมค่อนเดนเซอร์ชุดนี้เป็นวงจรที่มีอุปกรณ์ไม่  
มากขนาดกระหัดรัด เนื่องจากวงจรมีปรีไมค์และใช้ไมค์แบบค่อนเดน-  
เซอร์ ดังนั้นวงจนี้จึงมีความไว้วสูงกว่าธรรมดาก็อคด้วย

#### ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 9 โวลต์ดีซี
- กินกระแสสูงสุดประมาณ 5 มิลลิแอมป์
- ขนาดแพนวงจรพิมพ์ : 0.67 x 1.50 นิ้ว

#### การทำงานของวงจร

TR1 ต่อเป็นวงจรขยายแบบคลาส A สัญญาณจาก MIC จะผ่าน C1 มาขา A ของ TR1 เพื่อทำการขยายสัญญาณ ออกทางขา C ของ TR1 สัญญาณที่ทำการขยายแล้วจะผ่าน C2 ไปที่จุด OUT ตัว R1 จะทำหน้าที่เป็น R โหลดของ MIC ตัว C3 ทำหน้าที่บypassความถี่สูง

#### การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกแสดงไว้ในรูปที่ 2 ใน การประกอบวงจรควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอด ตาม ด้วยตัวต้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีหัวต่างๆ เช่น ไดโอด, คาปิซิเตอร์แบบอิเล็กทรอยไดโอด และทรานซิสเตอร์ เป็น ตน ควรใช้ความระมัดระวังในการประกอบวงจร ก่อนการใส่อุปกรณ์ เหล่านี้จะต้องหัวหัวที่แผ่นวงจรพิมพ์ทั้งอุปกรณ์ที่ต้องกัน เพราะ ถ้าหากใส่กลับหัวหัวแล้ว อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการ ถูกและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 แล้ว ในการบัดกรีให้ใช้ หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตะกั่วบัดกรีที่มีอัตราส่วนของ ดีนูกและตะกั่วยุ่รุระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ ภายในตะกั่วด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ ทำการตรวจสอบความถูกต้องอีกรั้งหนึ่ง เพื่อให้เกิดความมั่นใจแก่ ตัวเราเอง แต่ถ้าเกิดใส่อุปกรณ์ผิดตำแหน่ง ควรใช้ที่ถูกต้องหรือลด ชั้นตะกั่ว เพื่อนองค์ความเสียหายที่อาจจะเกิดกับสายวงจรพิมพ์ได้ สำหรับไมค์ค่อนเดนเซอร์ ก่อนใส่ต้องคุยกันให้ถูกต้องด้วย

#### การทดสอบ

ให้นำจุด OUT ของปรีไมค์ไปต่อ กับเครื่องขยาย โดยจะต้องก่อน โทน-คอนโทรล จ่ายไฟเข้าวงจรโดยผ่านสวิตช์ เปิดสวิตช์เพื่อจ่ายไฟ เข้าวงจร ค่อยๆ หมุนวอลุ่มที่เครื่องขยายเสียงขึ้นและทดลองพูดที่ ตัวไมค์ เสียงที่เราพูดจะถูกขยาย ขยายเสียงออกลำโพง

#### การนำไปใช้งาน

เมื่อนำไปใช้งาน หากเกิดอาการหวิด-หอน ให้นำไมค์ให้ห่างกับ ลำโพง แต่ถ้าห่างจริงปดคือแล้วจะมีความไว้วสูงเกินไป อาจต้อง C4 ออกหรือลดค่าให้ต่ำลง些ได้ เพื่อลดเกณฑ์การขยาย

## วงจรปรีพรมไมค์ค่อนเดนเซอร์

### CONDENSER MIC WITH PRE-AMP

CODE 648

LEVEL 1

This easy constructed preamplifier circuit incorporates a condenser microphone. The output of the FK648 is designed to suit the input requirements of most audio amplifiers.

#### Technical data

- Power supply : 9 VDC
- Electric current consumption : 5mA. (max.)
- IC board dimension : 0.67 in x 1.50 in.

#### How does it work

TR1 is connected as class-A amplifying circuit. The sound signal from the microphone passes through C1 and enters leg B of TR1 to amplify the signal out of its leg C. The amplified signal will pass through C2 and going to point OUT. R1 will serve as load R of the microphone. C3 will bypass the high frequency for the condenser microphone. Be sure to check whether the legs are correctly installed.

#### Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

#### Testing

Connect the pre-microphone at point OUT to the amplifier (prior to the tone control). Turn on the switch to supply power to the circuit. Gradually increase the volume of the amplifier and test speaking with the microphone. The sound will be amplified and depart from the loudspeaker.

#### Application

If there is a feedback noise from the loudspeaker, just turn the microphone away from the loudspeaker. In case the circuit is connected and it becomes too sensitive, C4 may be removed or reduced in order to decrease its amplification.

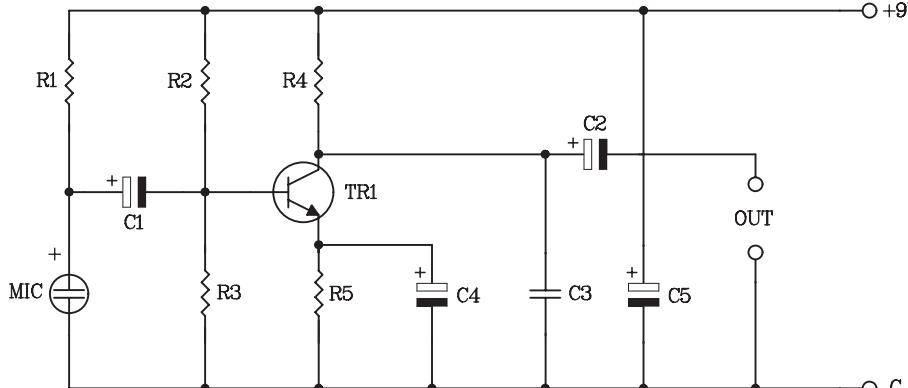


Figure 1. The Condenser MIC with Pre-amp Circuit

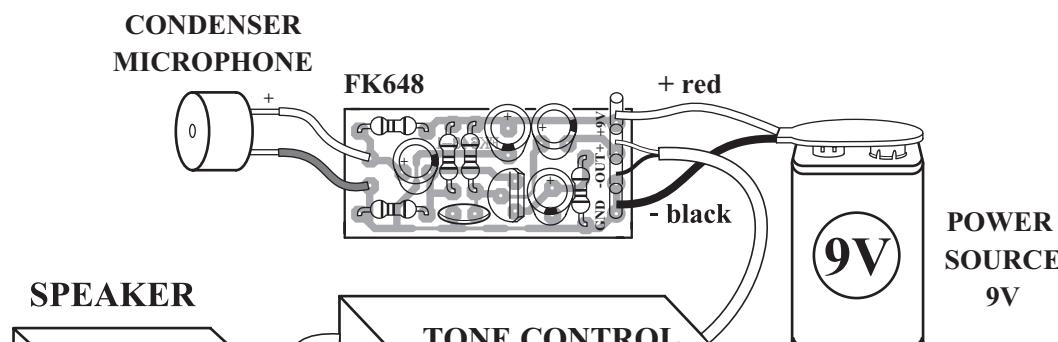


Figure 2.  
Circuit Assembling

NO.1

Figure 3. Installing the components

