



# FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรไฟวิ่งซึ่งติดต่อ LED วงอยู่ในรูปของลูกศร โดยในการกระพริบให้เป็นรูปลูกศรจะกระพริบอยู่ 3 จังหวะด้วยกัน วงจรนี้เหมาะสมที่จะนำไปประยุกต์ใช้งานในรูปแบบทางๆ เช่น นำไปประดับเพื่อความสวยงาม, นำไปใช้เป็นไฟทึ้งทางข้ามอุบัติเหตุ ไฟเลี้ยวในรถยนต์ เป็นต้น

#### ข้อมูลทางด้านเทคนิค

- ไฟแหล่งจ่ายไฟขนาด 9-12 โวลต์ดีซี
- กินกระแสสูงสุดประมาณ 70-120 มิลลิแอมป์
- มีตัวปรับความเร็วในการกระพริบ
- ขนาดเมษายน้ำจารพิมพ์ : 2.84 x 2.12 นิ้ว

#### การทำงานของวงจร

วงจรนี้ดัดเป็นวงจรกำเนิดความถี่ประจำหนึ่ง ประกอบด้วย TR1, TR3 และ TR5 ทำหน้าที่ผลิตความถี่ ซึ่งจะทำงานเป็นจังหวะ 3 จังหวะ โดยมีอุปกรณ์คล้ายๆ กัน 3 ชุด ต่อร่วมกันอยู่โดย R2, R8, R15 และ C1-C3 ทั้ง 3 ชุด เป็นตัวกำหนดความเร็วในการกระพริบของ LED TR4 และ TR2 จะทำหน้าที่เป็นตัวกลับเฟสและไดรฟ์ไฟ LED ส่วน R3-R5 และ R9-R12 ทำหน้าที่เป็น LOAD เพื่อลดกระแสไฟกับ LED D3 จะเป็นตัวช่วยให้ในชุดที่ 1 ติดค้าง ในขณะที่ชุดที่ 2 ทำงาน

#### การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกแสดงไว้ในรูปที่ 2 ใน การประกอบวงจร ควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวต้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ เช่น ไดโอด, คากาป้าสิสเตอร์แบบบอร์ดทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบวงจร ก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ขั้วที่แผ่นวงจรที่มีพกันตัวอุปกรณ์ให้ตรงกัน เพราะหากไม่ได้ อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูขั้ว และการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และใน การบัดกรีให้หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตะเกียบดัดกรีที่มีอัตราส่วนของดินกุ๊ดและตะกั่วอยู่ระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ภายในตะเกียบดัดกรีที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง เพื่อให้เกิดความมั่นใจเกิดตัวเรื่อง แต่หากเกิดอุปกรณ์ติดค้าง ควรใช้คุณตัวหัวอวลดชั้บตัวกับเพื่อป้องกันความเสียหายที่อาจจะเกิดกับลักษณะพิมพ์ได้

#### การทดสอบ

ทำการจ่ายไฟตรงขนาด 9 โวลต์ ต่อเข้าวงจร จากนั้นไฟที่ LED จะเริ่มติด โดยจะเริ่มติดที่ 4 แถวหลังก่อน ต่อมาจะติดในส่วนที่เหลือในจังหวะสุดท้าย LED จะดับทุกดวง และก็จะไปเริ่มที่จังหวะแรกใหม่ จะเป็นอย่างนี้ไปเรื่อยๆ ถ้าเป็นไปตามนี้ แสดงว่า วงจรพร้อมใช้งานแล้ว ต้องการใช้เป็นเวลานานก็สามารถใช้อแดปเตอร์ขนาด 9-12 โวลต์ได้

## วงจรไฟวิ่งซึ่งติดต่อ LED 21 ดวง

### ARROW CHASING LIGHT

CODE 149

LEVEL 1

This arrow shaped flasher features a matrix of 21 LEDs that are sequenced through in three steps of 7 LEDs in an attention grabbing display. The FK149 will find application in crowd or traffic direction control, retail point-of-sale highlighters, decorations and portable emergency units.

#### Technical data

- Power supply : 9-12VDC.
- Electric current consumption : 70-120mA max.
- IC board dimension : 2.84 in x 2.12 in.

#### How does it work

This is a 3 steps variable-frequency multivibrators circuit (consists of TR1, TR2 and TR3). There are 3 alike components sets being jointly connected and having 3 sets of R2, R8, R15 and C1 to C3 for controlling the flashing speed of LEDs. TR4 and TR2 will reverse the phase and drive LEDs for brightness. R3-R5 and R9-R12 will act as a load reducer for LEDs. D3 will act as a helper for set 1 to be permanently lit while the second set working.

#### Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

#### Testing

Supply 9VDC to the circuit, LEDs will start being lit. LEDs of the first 4 back rows will be lit first and later for the rest. At the last step, all LEDs will be off and then restarted at the first step again. Those above results will show that the circuit is workable. For longer operation, it is recommended to use a 9-12V adaptor.

Figure 1. Arrow Chasing Light Circuit

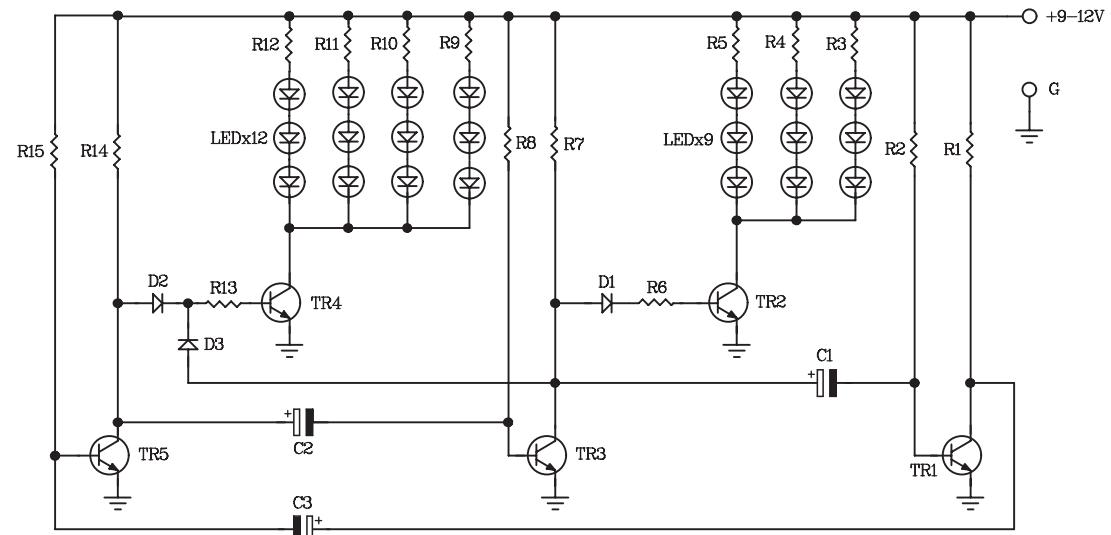


Figure 2. Circuit Assembling


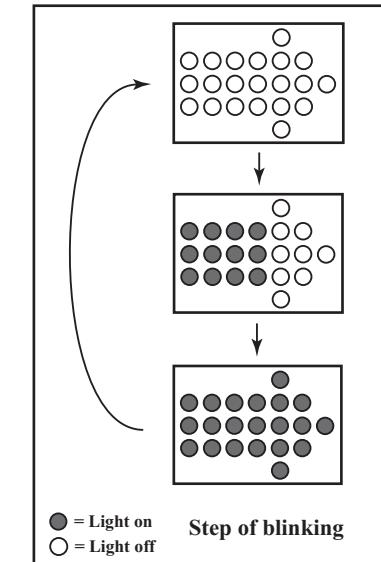
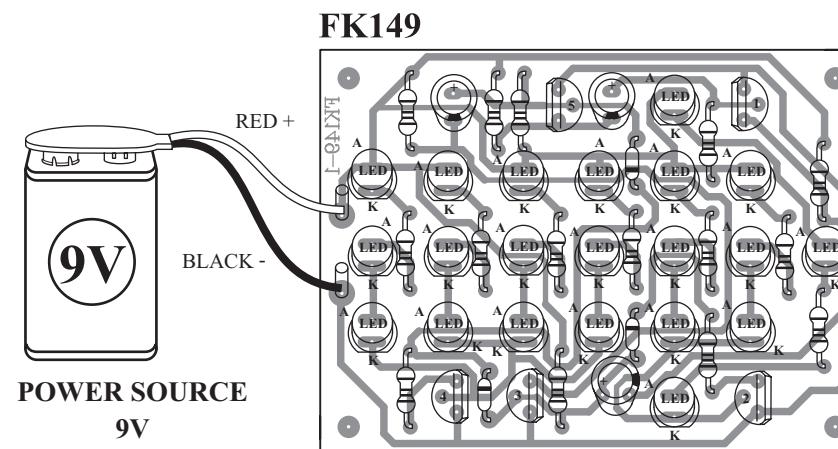


Figure 3. Installing the Components

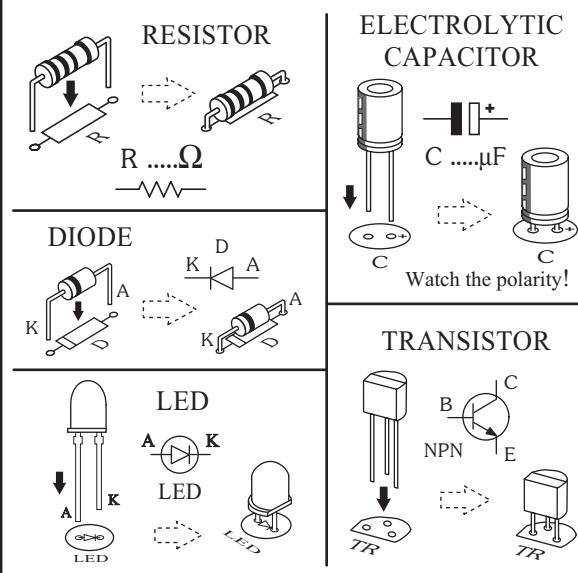

#### NOTE:

FUTURE BOX FB03 is suitable for this kit.