



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรแสงหิ้งห้อย กระพริบตอนกลางคืน
FIREFLY LIGHT (NIGHT ACTIVATE)
CODE 167

ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 3 โวลต์ดีซี
- กินกระแสสูงสุดประมาณ 0.20 มิลลิแอมป์ (ขณะยังไม่ทำงาน), 11 มิลลิแอมป์ (ขณะทำงาน)
- ใช้ตัวโพโตทรานซิสเตอร์เป็นเซ็นเซอร์ตัวจับแสง
- ขนาดแผ่นวงจรพิมพ์ : 1.57 x 1.18 นิว

การทำงานของวงจร

ในสภาวะปกติ เมื่อมีแรงมาต่อวงจรที่ตัวโพโตทรานซิสเตอร์ ความต้านทานภายในจะมีค่าต่ำลง ทำให้ TR1 ทำงาน โดย TR1 จะไปทำการคายประจุ C1 ลงกราวน์ วงจรจึงไม่ทำงานและ LED1 จึงไม่ติดตามไปด้วย แต่เมื่อได้กิตามที่ไม่มีแรงมาต่อวงจรที่ตัวโพโตทรานซิสเตอร์ ความต้านทานภายในก็จะสูง ทำให้ TR1 ไม่ทำงาน C1 จึงทำการคายประจุไฟผ่านทาง R5 จนกระทั่งแรงดันที่ขา E ของ TR2 มีค่าสูงกว่าที่ขา B ของ TR2 ประมาณ 0.6 โวลต์ TR2 จึงทำงาน รวมทั้ง TR3 และ LED1 ด้วย ในขณะนี้แรงดันที่ C1 จะถูกคายประจุโดย ผ่าน D1 และ TR3 ลงกราวน์ จนกระทั่งแรงดันที่ขา E ของ TR2 ต่ำกว่าขา C ของ TR2 ทรานซิสเตอร์ TR2 และ TR3 จึงหยุดทำงาน LED1 ก็จะหยุดทำงานตามไปด้วย และการทำงานก็จะวนกลับไปทำงานเหมือนกับครั้งแรก

แรก

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกແສດງไว้ในรูปที่ 2 ใน การประกอบจะควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วย ตัวต้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ เช่น ไดโอด, แคปซิลเตอร์แบบอิเล็กทรอลิคและทรานซิสเตอร์ เป็นต้น การใช้ความระมัดระวังในการประกอบจะก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ขั้วที่แผ่นวงจรพิมพ์กับตัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับขั้วแล้ว อาจทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูขั้วและ การใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และ หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้วให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง เพื่อให้เกิดความมั่นใจแก่ตัวเราเอง

การทดสอบ

ก่อนทำการจ่ายไฟ ให้หันตัวโพโตทรานซิสเตอร์ ไปทางแสงสว่าง จากนั้นจึงจ่ายไฟเข้าวงจร ในขณะนี้ LED1 จะยังไม่กระพริบหาวสุด ที่นิ่งมากครอบที่ตัวโพโตทรานซิสเตอร์ สังเกต LED1 จะเริ่มติดกระพริบเป็นจังหวะ ถ้าต้องการให้กระพริบเร็วกว่านี้ ให้ทำการลดค่าของ C1 ลง

Just like real fireflies that come out at night and flash their lights, the photo transistor in the FK167 senses the dark and turns on the LED Flasher. The FK167 is designed to drive a red LEDs; however, other colors may be incorporated to prove that there is sufficient voltage to drive them. The FK167 is an excellent science show demonstrator or outdoor decoration at parties.

Technical data

- Power supply : 3VDC.
- Electric current consumption : 0.2mA (standby), 11mA (working)
- Light sensor : a photo-transistor.
- IC board dimension : 1.57 in x 1.18 in

How does it work

In normal condition where the light illuminates the phototransistor, the internal resistance decreases and TR1 discharges C1 to the ground, so the circuit is idle and LED1 does not flash. Once no illumination onto the phototransistor, the internal resistance becomes high and TR1 stops working, C1 then charges through R5 until the voltage at leg E of TR2 is higher than that of leg B by 0.6 volt and it starts working, so do TR3 and LED1. At this point the voltage at C1 is discharged through D1 and TR3 to the ground. Once the voltage at leg E of TR2 is lower than that of leg C of TR2, then TR2 and TR3 stop working and neither does LED1. The circuit will repeat this cyclic order again and again.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

Set the phototransistor to the direction of coming-in light before energizing the circuit, LED1 will not blink. Cover the phototransistor with an opaque object and observe LED1; it will start blinking in a rhythmic fashion. If the slower frequency is required, reduce the capacity of C1.


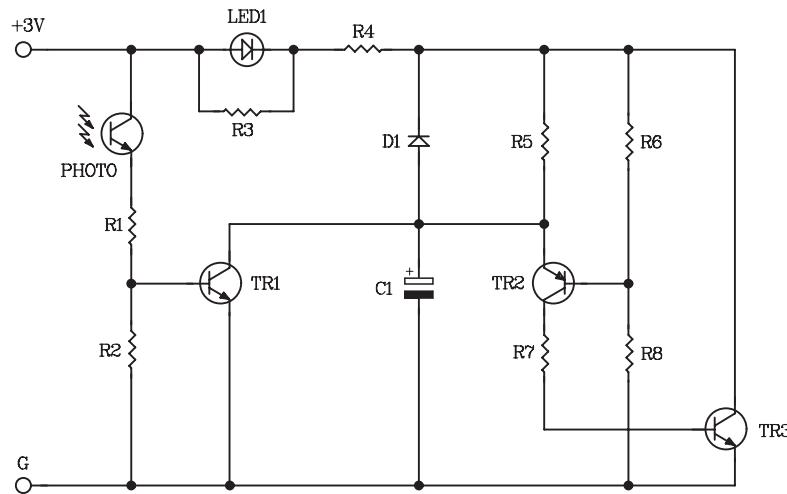


Figure 1. The Firefly Light (Night Activate) Circuit


Figure 2. Circuit Assembling

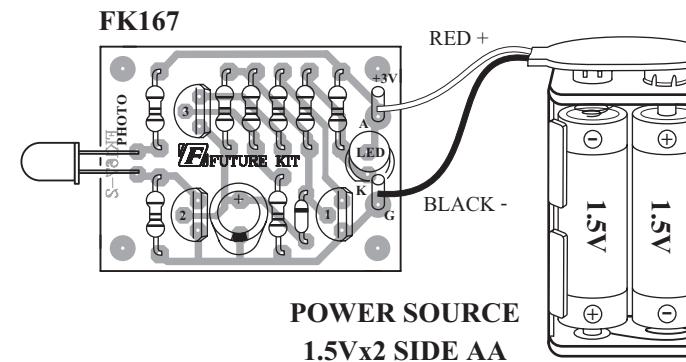

POWER SOURCE
1.5Vx2 SIDE AA

NO.2

Figure 3. Installing the components

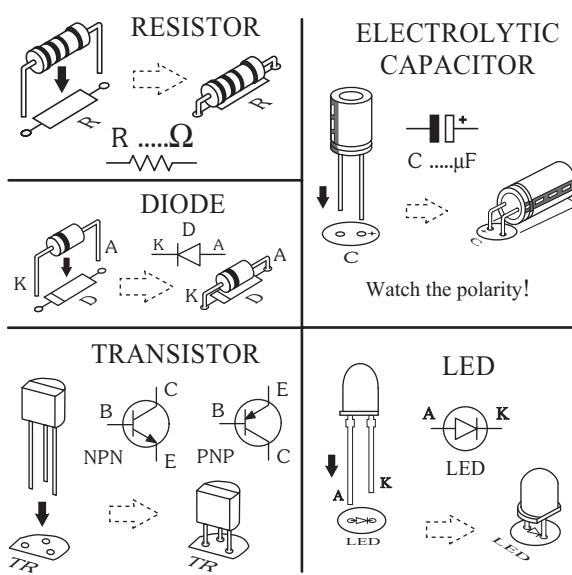

NOTE:

FUTURE BOX FB17 is suitable for this kit.