



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรไฟเร้นดับเพลิง
FIRE SIREN
CODE 233
LEVEL1

วงจรไฟเร้นดับเพลิงนี้ เป็นวงจรกำเนิดความถี่แบบง่ายๆ ใช้อุปกรณ์อย่างง่ายๆ สำหรับเด็กที่เริ่มประกอบใหม่

ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 9 โวลต์ดีชีз
- กินกระแสสูงสุดประมาณ 20 มิลลิแอมป์
- ใช้กับลำโพงขนาด 8 โอห์ม 0.25 วัตต์
- ขนาดแผ่นวงจรพิมพ์ : 1.07 x 1.32 นิ้ว

การทำงานของวงจร

TR1, TR2, R3, C2 และลำโพงต่อเป็นวงจรกำเนิดความถี่ โดยความถี่จะถูกควบคุมที่ขา B ซึ่งที่ขา B นี้จะต่อผ่าน R2 เพื่อรับแรงไฟฟ้าไปอัลตร้าโซนิกที่ C1 จะได้รับการชาร์จผ่าน R1 และสวิตช์ทำให้แรงไฟที่ C1 ค่อยๆ เพิ่มขึ้น ชุดกำเนิดความถี่จะทำงานโดยความถี่จะค่อยๆ สูงขึ้นตามแรงดันที่ตกครوم C1 เมื่อ C1 ชาร์จไฟถึงจุดหนึ่ง เสียงจะมีความถี่คงที่ เมื่อเราปล่อยสวิตช์แรงไฟที่ค้างอยู่ใน C1 จะค่อยๆ ลดลง จึงทำให้ความถี่ลดลงตามลำดับและเสียงจะหยุด เมื่อ C1 ดิสชาร์จไฟต่ำกว่า 0.6 โวลต์โดยเสียงที่ได้จะมีลักษณะคล้ายเสียงไฟเร้นดับเพลิง

การประกอบวงจร

รูปการลงอุปกรณ์แสดงไว้ในรูปที่ 2 ในการประกอบวงจร ควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวต้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ เช่น ไดโอด ค่าปั๊สเตอร์แบบบิเล็กทรอนิกส์และทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบวงจร ก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้ขั้วที่แผ่นวงจรพิมพ์กับตัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับข้ามแล้ว อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการตัดขั้วและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และ ในการบัดกรีให้ใช้หัวแร้งขนาดไม่เกิน 40 วัตต์ และใช้ตะเก็บดกรีที่มีอัตราส่วนของดีบุกและตะเก็บอยู่ระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ภายในตะเก็บด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง แต่ถ้าเกิดใส่อุปกรณ์ผิดตำแหน่ง ควรใช้ที่คูดตะกั่วหรือลวดซับตะกั่ว เพื่อป้องกันความเสียหายที่อาจจะเกิดกับลายวงจรพิมพ์ได้

การทดสอบ

ให้ทำการต่ออุปกรณ์ต่างๆ ตามรูปที่ 2 จ่ายไฟขนาด 9 โวลต์ เข้าที่วงจร ในตอนนี้วงจรจะต้องไม่มีเสียงออกทางลำโพง ให้กดสวิตช์ลงไว้จะได้ยินเสียงค่อยๆ สูงขึ้นคล้ายเสียงไฟเร้นจนถึงระดับหนึ่ง เสียงจะคงที่ไปปล่อยสวิตช์ตอนนี้เสียง จะค่อยๆ ต่ำลงและหยุดในที่สุดเสียงที่ได้จะเหมือนกับเสียงรถไฟเร้นดับเพลิง

วงจรไฟเร้นดับเพลิง

FIRE SIREN

CODE 233

Our most popular and practical small kit, the FK233 is a great favorite of boys of all ages. Several electronic functions such as sound generation, push button control of sound rise and fall control are quickly realized in this economical project. The kit comes complete with 8 ohm 0.25W speaker and alarm systems.

Technical data

- Power supply : 9VDC.
- Electric current consumption : 20mA (max.)
- It suits with an 8-ohm/0.25-watt loudspeaker.
- IC board dimension : 1.11 in x 1.28 in.

How does it work

TR1, TR2, R3, C2 and the loudspeaker are connected as frequency generating circuit which is controlled at leg B through R2 to gain the voltage and bias TR1. Once the switch is pressed C1 will be charged via R1 and the voltage at C1 will gradually increase. The frequency generating unit will work and its frequency will gradually increase pursuant to the drop of voltage across C1. At a point when C1 is fully charged its sound frequency will be constant and when the switch is released the existing voltage will gradually drop and the frequency will gradually decline and finally stop when C1 discharge lower than 0.6 volt, resulting a sound similar to that of the fire siren.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

Connect the component as per Fig. 3 and supply 9 VDC to the circuit. Now the circuit shall not make any sound from the loudspeaker. Keep pressing the switch the sound will be higher and higher resembling the siren sound, and up to a point the frequency will become constant, so release the switch. Now the sound will gradually lower and finally stop.

Figure 1. The Fire Siren Circuit

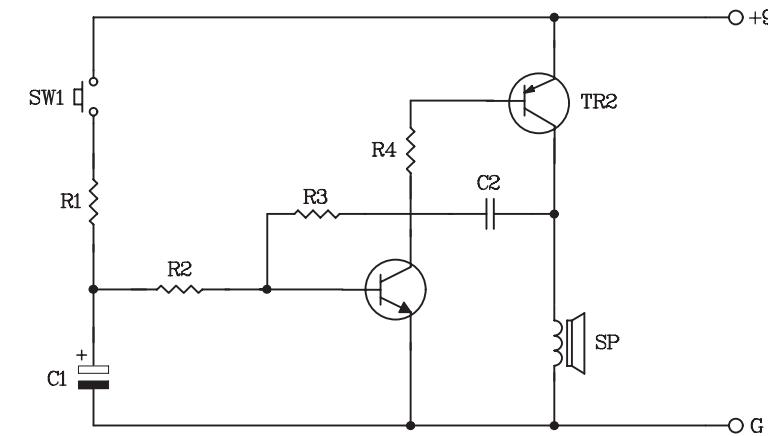


Figure 2. Circuit Assembling


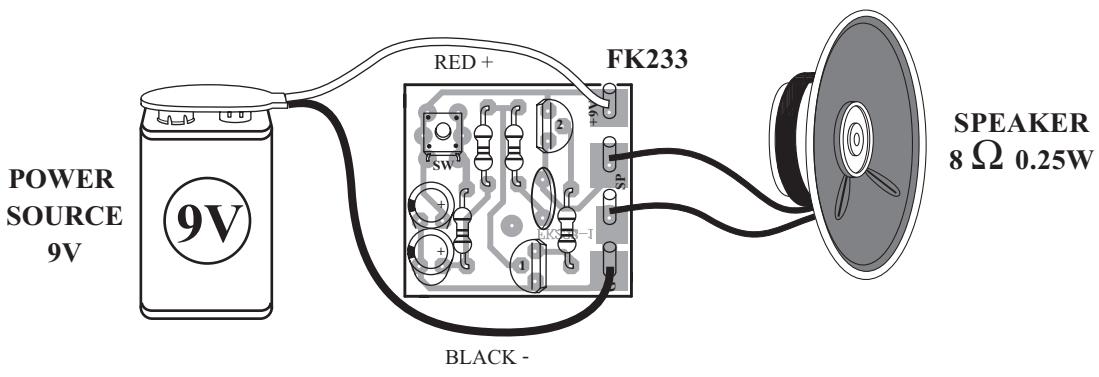


Figure 3. Installing the components

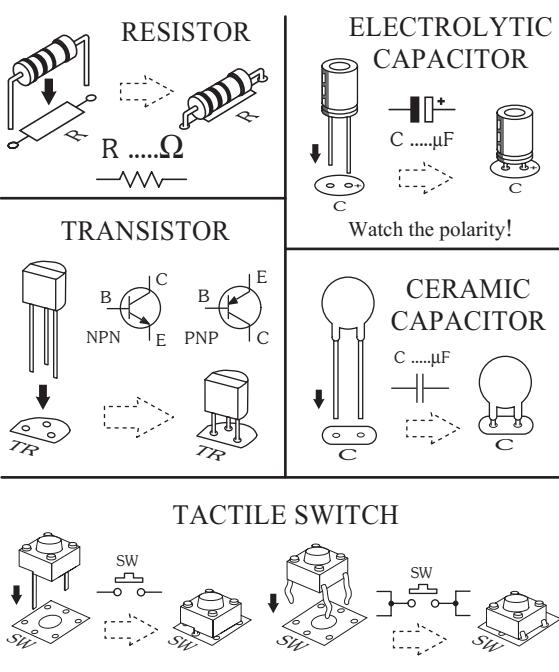

NOTE:

FUTURE BOX FB03 and FB17
are suitable for this kit.