



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงศ์ไมค์โลย FM ชุดนี้ เป็นวงศ์ไมค์โลยที่เขียนลายปรินท์เป็นคอกย์ในวงจรโซลูชันดังนั้นจึงทำให้การประกอบสร้างได้ง่าย

ข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 3 โวลต์ดีซี
- กินกระแสสูงสุดประมาณ 10 มิลลิแอมป์
- ความถี่ที่ส่งอยู่ในย่าน 88 เมกกะเฮتز
- ขนาดแพนแองจรพิมพ์ : 1.64 x 1.06 นิ้ว

การทำงานของวงจร

แผนผังวงจรแสดงในรูปที่ 1 ไมค์ค่อนเดนเซอร์จะทำหน้าที่รับเสียงที่พูดเข้าไป โดยภายในตัวไมค์จะมีเฟกบยาส์-آلเสียงที่ทำการขยายจากไมค์จะส่งผ่าน C2 ไปเข้าขา B ของ TR1 ซึ่ง TR1 จะทำหน้าที่กำนิดความถี่คลื่นวิทยุและเป็นตัวผสมเสียงกับความถี่วิทยุที่สร้างขึ้น สำหรับความถี่ที่สร้างจะขึ้นอยู่กับทริมเมอร์และค่าความถี่ที่ตั้งค่าไว้ใน IC ของ TR1 จะต่อไปน้ำเสียงจะถูกส่งออกอากาศ ต่อไป

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกแสดงไว้ในรูปที่ 2 ในการประกอบวงจรควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวด้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้วต่างๆ เช่น ไดโอด ค่าปั๊สเตอร์แบบอิเล็กทรอนิกส์และทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบจะรองรับการใส่อุปกรณ์เหล่านี้จะต้องหัวใจที่แผ่นวงจรพิมพ์กับตัวอุปกรณ์ให้ตรงกัน เพราะหากนำไปติดผิดกัน แล้วอาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูแลและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และ

การทดสอบ

ให้ต่อไฟ 3 โวลต์ โดยขั้วบวกต่อที่ +3V. ขั้วนegต่อที่ขั้ว G สำหรับอุปกรณ์ ANT ให้ต่อ กับสายบัดกรีที่จุด ANT โดยจะต้องบุน้ำยาออก ก่อน และบัดกรีตามขั้นตอนนี้ยาออกจะบัดกรีไม่ติด หมุนสถานีวิทยุ FM ไปที่ตำแหน่ง 88MHz ใช้ไขควงที่เป็นพลาสติกอยๆ ปรับทริมเมอร์จนเมื่อเสียงหวิดหอนออกทางวิทยุ และทดสอบฟูดิส์ไมค์ จะได้ยินเสียงที่พูดออกทางลำโพงวิทยุ แต่หากลองแล้วไม่มีเสียงออกลำโพง ให้หมุนคลื่นวิทยุไปประมาณ 100MHz ถ้ายังไม่ได้อึกให้หมุนคลื่นวิทยุไปจนสุด 108MHz และทดสอบปรับดูอีกรั้ง

วงศ์ไมค์โลย FM 3 โวลต์

FM WIRELESS MIC 1 STATE (LOW VOLTAGE)

CODE 701 LEVEL 1

The FM wireless microphone is coil imprinted in resonant circuit so that it is easy to assemble.

Technical data

- Power supply : 3VDC.
- Electric current consumption : 10mA. (max.)
- Transmitting frequency: approx. 88 MHz (adj.)
- IC board dimension : 1.64 in x 1.06 in

How does it work

Figure 1 presents the circuit diagram. This circuit utilizes a condenser MIC to work the reception function. There is an amplifier stage in microphone. The amplified signal will be transmitted through C2 to the base of TR1 which oscillates the radio frequency and mix the two frequency together. The oscillated frequency is related to the trimmer and imprinted coil. The collector of TR1 is connected to an antenna to be on air.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig. 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

Connect the power supply 3 volts to "+3V" and "G" point. Remove the solution before solder "ANT" point with coil. Then adjust the FM TUNER to 88MHz. Slightly adjust the trimmer by using a plastic screw until there is a horn sound throughout the radio. Talk to the microphone. The sound will be heard through the radio speaker. If 88MHz is unpractical, adjust FM TUNER to 100MHz or at last 108MHz and test again.


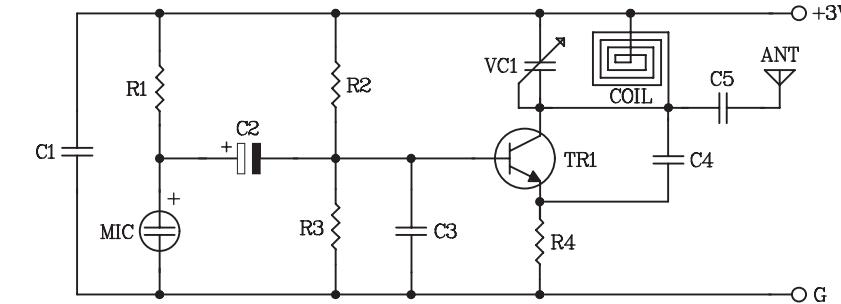



Figure 1. The FM Wireless MIC 1 State (Low Voltage) Circuit

Figure 2. Circuit Assembling

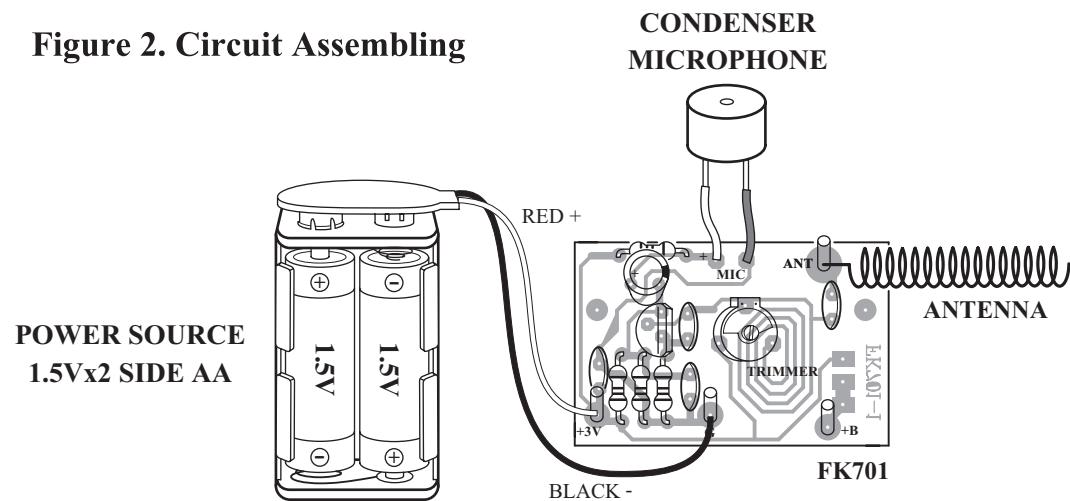

NO.1

Figure 3. Installing the components

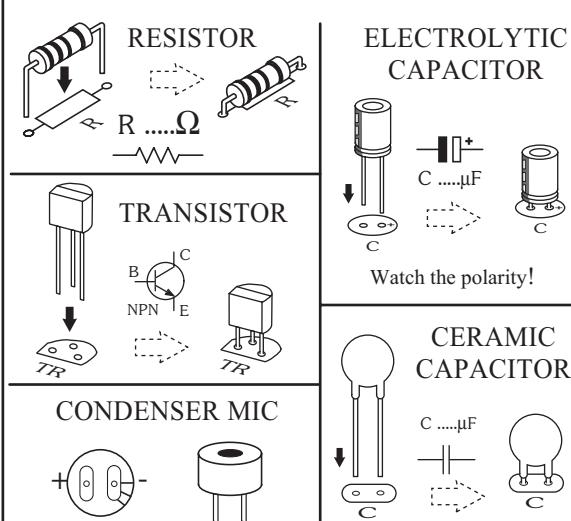

NOTE:

FUTURE BOX FB08 is suitable for this kit.