



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรปรับไฟ 0-12 โวลท์ ชุดนี้ จัดเป็นวงจรเร็คเกลตันิดหนึ่งที่มีการทำงานแบบง่ายๆ คุณภาพพอใช้ราคายังถูก แต่ให้ประโยชน์ในการใช้งานคุ้มค่าที่เดียว ก่อราก็สามารถใช้งานเพิ่มขึ้นกับแหล่งจ่ายไฟธรรมดามีเม็ด เช่น แบตเตอรี่หรือหม้อแปลงไฟให้สามารถปรับโวลท์ได้ตลอดยานด้านอินพุตของวงจร หากเราป้อนไฟที่เร็คคิฟายจากไฟ AC 12 โวลท์ ก็สามารถปรับเอาท์พุตได้ตั้งแต่ 0-12 โวลท์ วงจนีตัวปรับจะใช้เกล็อกม้าหรือวอลลูมแบบมีแกนกีดข้อมูลทางด้านเทคนิค

- ใช้แหล่งจ่ายไฟขนาด 12-15 โวลต์ดีซี
- สามารถปรับแรงดันเอาท์พุตได้ 0-12 โวลท์
- สามารถจ่ายกระแสได้สูงสุด 1 แอมป์ (ใช้หม้อแปลง 1.5 แอมป์)
- ขนาดแพนวงจรพิมพ์ : 1.28x1.22 นิ้ว

การทำงานของวงจร

ด้านอินพุตของวงจรเราจะจ่ายไฟที่ประมาณ 12 โวลต์ขึ้นไป เทากำา C ของ TR1 และขณะเดียวกันจะมี R1 กับ VR1 ตอบเป็นวงจรแบบแรจไฟและมี C 33 ไมโครเป็นตัวฟิลเตอร์ไฟให้เรียบยิ่งขึ้น เมื่อเรามุน VR1 จะไฟเปลี่ยนแปลงตั้งแต่ 0-10 โวลท์ แรงไฟที่จุดนี้ยังไม่สามารถนำไปใช้งานได้ เพราะมันจ่ายกระแสได้ต่ำมากดังนั้นเราจึงต้องเข้ากับ TR2 และ TR1 เพื่อย้ายกระแสให้มากพอ คือ ประมาณ 1 แอมป์ ทั้งนี้ TR1 จะเป็นประเภททันกำลังได้สูง เวลาใช้งาน ควรติดแผ่นระบายความร้อนให้กับมัน ด้วยแรจไฟที่ผ่านการปรับโวลท์และขยายกระแสแล้วจะออกทางขา E ของ TR1 ซึ่งที่จุดนี้เราจะได้กระแสไฟที่ปรับได้ตั้งแต่ 0-12 โวลท์ โดยมี C2 ไมโครเป็นฟิลเตอร์อีกชั้นหนึ่ง

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายนอกแสดงไว้ในรูปที่ 2 ใน การประกอบวงจรควรจะเริ่มจากอุปกรณ์ที่มีความสูงที่น้อยที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วย ตัวต้านทานและໄล์ความสูงไปเรื่อยๆ สำหรับอุปกรณ์ที่มีขั้ว เช่น ไดโอด, คากาซิสเตอร์แบบมอลิกทรอล์, และทรานซิสเตอร์ เป็นต้น

การทดสอบ

เมื่อประกอบเสร็จ ให้ลองจ่ายไฟเข้าที่ INPUT 12-16V และ ใช้โวลต์มิเตอร์วัดที่จุดเอาท์พุต ลองปรับ VR1 และสังเกตค่าโวลท์ที่มีเมตร ควรจะอ่านได้ตั้งแต่ 0 โวลท์ ขึ้นไป จนเกือบถึงค่าโวลท์ที่จ่ายเข้า

วงจรปรับลดไฟ DC 0-12V.

DC REGULATOR 0-12V

CODE 807

LEVEL 1

It is a sort of regulating circuit for 0-12VDC appliances. Although it is not expensive and works simply but it is worth for use, especially in case it is added to the existing source of power supply e.g. battery or transformer because the voltage can be adjusted throughout the input range of the circuit. If we supply 12VAC to the transformer the output voltage can be continuously adjusted lower by a potentiometer/spindle pot.

Technical data

- Power supply : 12-15VDC.
- Voltage output : 0-12VDC (adjustable)
- Maximum load : 1A. (with 1.5A. transformer)
- IC board dimension : 1.28 in x 1.22 in

How does it work

Supply 12VDC to the right side of circuit input at leg C of TR1 and in the meantime R1 and VR1 share the voltage from it whereas C2 acts as filter to smoothen the current. Once VR1 is turned the voltage will vary continuously from 0 to 10 volts. The voltage at this point cannot be utilized because it supplies very low current. So we have to connect it to TR2 and TR1 to increase it up to 1A. TR1 shall be of high-voltage durable type. However, a heat repellent fin shall be attached to it at use. The adjusted voltage and the increased current will depart from leg E of TR1.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolytic capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

Test by supplying 12-16VDC to the circuit input. And measure the voltage with a voltmeter. Adjust VR1 and observe the voltmeter. The reading shall be greater than 0 volt up to a value near to the supplied voltage.


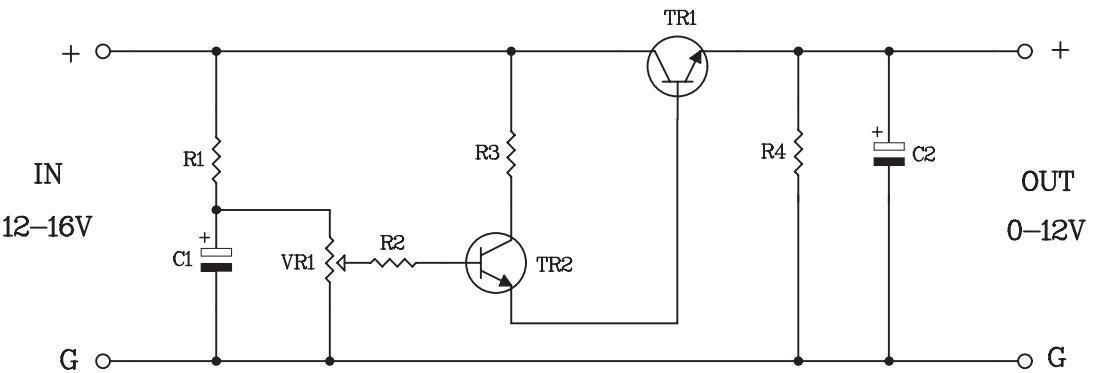



Figure 1. The DC Regulator 0-12V Circuit

Figure 2. Circuit Assembling

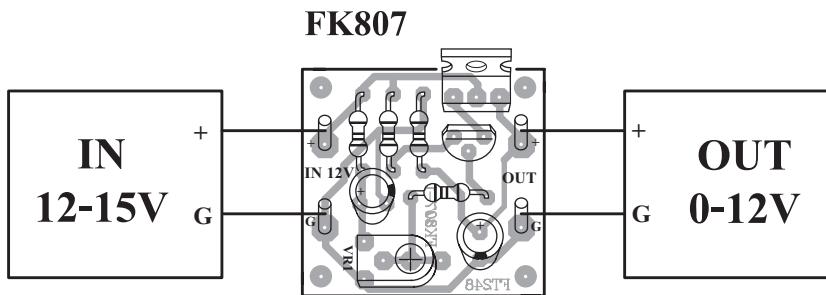

NO.1

Figure 3. Installing the components

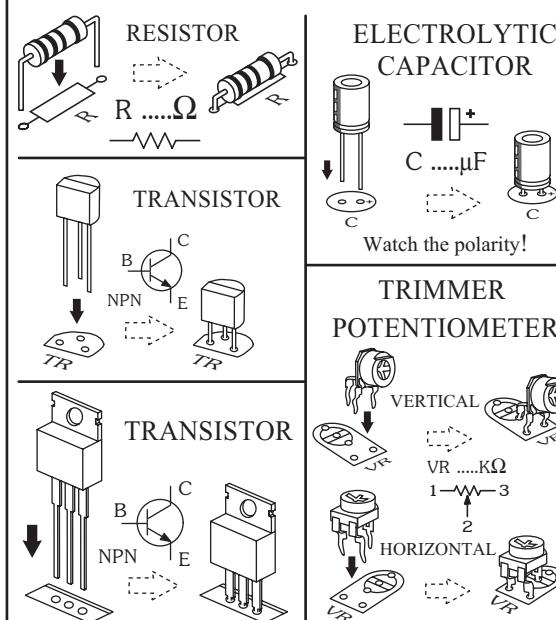

NOTE:

FUTURE BOX FB01 is suitable for this kit.